

# LED Interfacing and Resistor Calculation

---

## Understanding the Importance of Current-Limiting Resistors

When interfacing LEDs with Arduino pins, it's crucial to include current-limiting resistors in the circuit. LEDs have specific forward voltages and forward currents at which they operate optimally. Without a current-limiting resistor, excessive current can flow through the LED, potentially damaging both the LED and the Arduino pin.

## Calculating Resistor Values for Safe LED Operation with Arduino Pins

To calculate the current-limiting resistor value, you can use Ohm's Law:

$$R = (V_{\text{source}} - V_{\text{LED}}) / I_{\text{LED}}$$


Where:

- R is the resistance in ohms.
- V\_source is the source voltage (Arduino pin voltage, typically 5V).
- V\_LED is the forward voltage drop across the LED.
- I\_LED is the desired LED current.

Let's assume:

- V\_source = 5 volts (Arduino HIGH level voltage).
- V\_LED is the forward voltage of your LED (check the datasheet).
- I\_LED is the desired LED current (choose a safe value, e.g., 10-20 mA for standard LEDs).

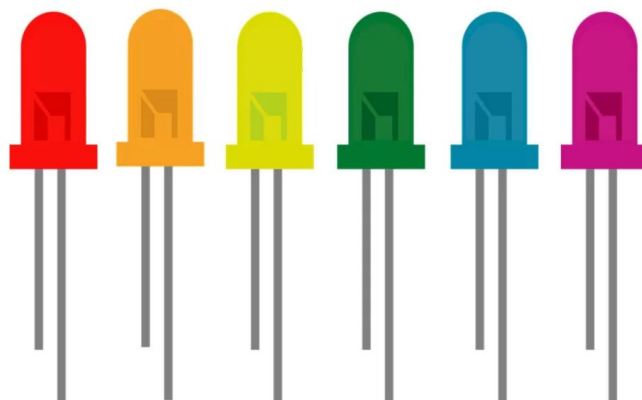Color, Forward Voltage (V) of standard LEDs



- Red: 1.7-2.0 V
- Orange: 2.0-2.2 V
- Yellow: 2.1-2.3 V
- Green: 2.2-2.4 V
- Blue: 3.0-3.3 V
- White: 3.0-3.4 V

**Example:**

Let's say you have an LED with  $V_f = 2.2 \text{ V}$  and  $I_f = 20 \text{ mA}$ , and you're using a  $9 \text{ V}$  power supply.

1.  $V_r = 9 \text{ V} - 2.2 \text{ V} = 6.8 \text{ V}$
2. Choose  $I_{\text{LED}} = 18 \text{ mA}$  (slightly below the maximum).
3.  $R = \frac{6.8 \text{ V}}{0.018 \text{ A}} \approx 377.78 \Omega$
4. Select a standard resistor value, e.g.,  $390 \Omega$ .
5. Verify power rating:  $P_{\text{resistor}} = 0.018 \text{ A} \times 6.8 \text{ V} \approx 0.1224 \text{ W}$ , so a  $0.25 \text{ W}$  resistor should suffice.

Choose a resistor close to  $390 \Omega$  with a power rating of  $0.25 \text{ W}$ , and you should be good to go.